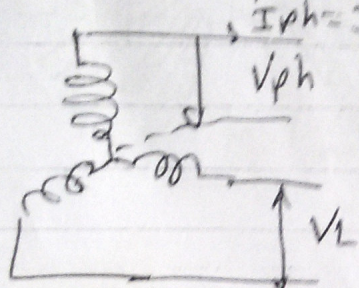


* Synchronous Machines *

Construction

a) - Stator [Armature]



the same of 3- ϕ I.M



star connection

$$V_{ph} = \frac{V_L}{\sqrt{3}}$$


$$I_{ph} = I_L$$

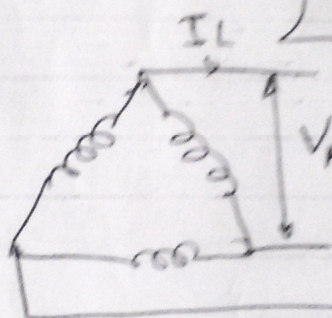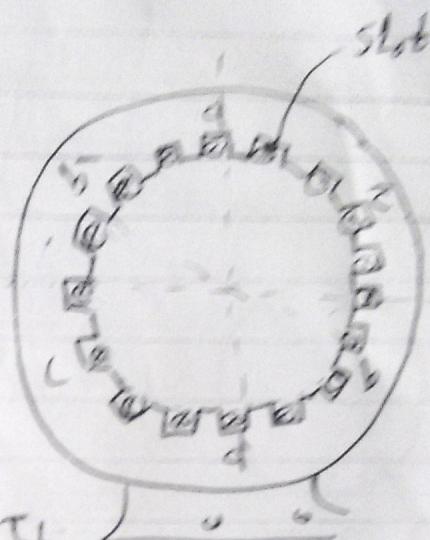

delta connection

b) - rotor [field winding]

1- Salient Pole rotor

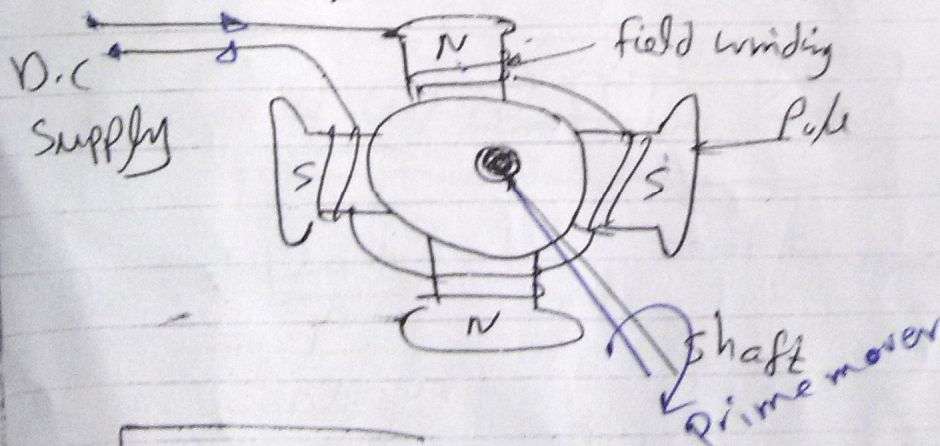


P 7/4

No. of Poles


- * air gap is non uniform
- * Mechanically weak
- * Used for low speed
- * Used for water turbine engines

2

2. Cylindrical rotor

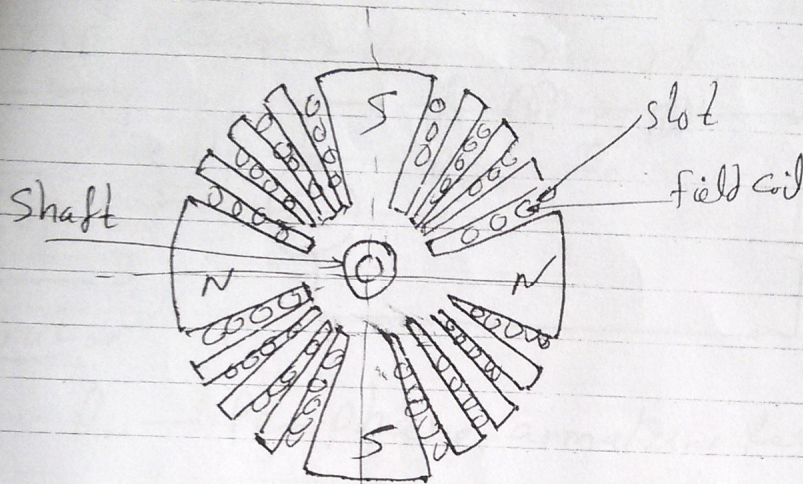

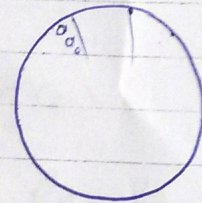- * air gap is uniform
- * mechanically robust
- * used for high speed



⊗ Working Principle

فكرة العمل

N_s as rotor \Rightarrow rotor \Rightarrow rotor \Rightarrow rotor

Armature \Rightarrow rotor \Rightarrow rotor \Rightarrow rotor

$$emf = N \frac{d\phi}{dt}$$


emf

$$E_{ph} = 4.44 \phi_m f T_{ph} K_w$$


no. of turns per phase $\Rightarrow E_{max}$

$$N_s = \frac{120 f}{P}$$

$$f = \frac{N_s P}{120}$$

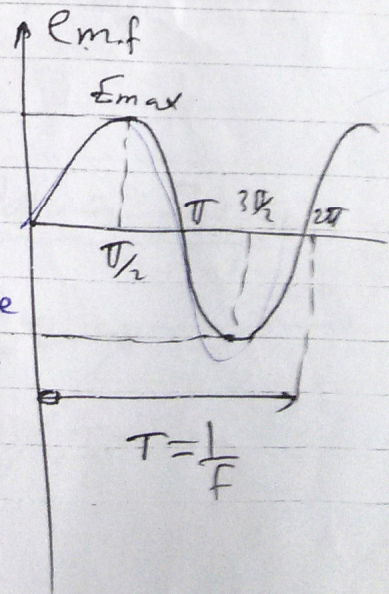

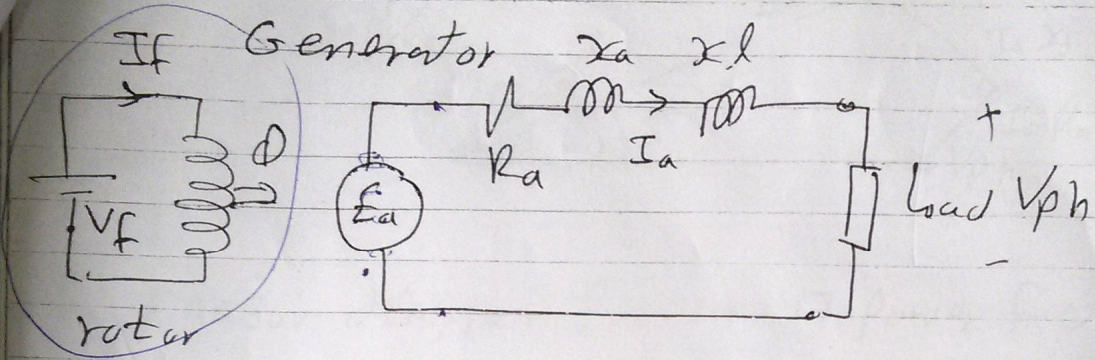
The per-phase equivalent circuit of synchronous



$R_a \rightarrow$ Per phase armature resistance


X_a — " " " Reaction Reactance
 X_l — " " " Leakage Reactance

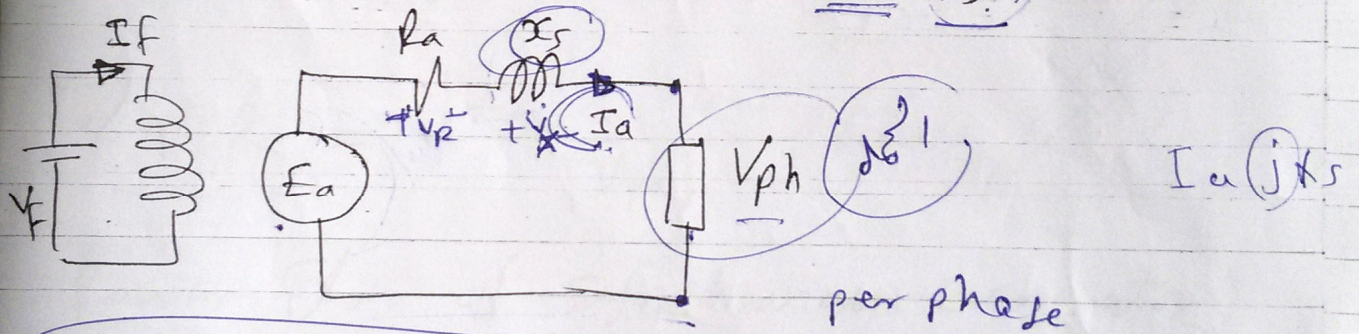$X_s \rightarrow$ Synchronous Reactance = $X_a + X_l$



$$E_a = V_{ph} + I_a(R_a + jX_s)$$


Phasor diagram for lag power factor

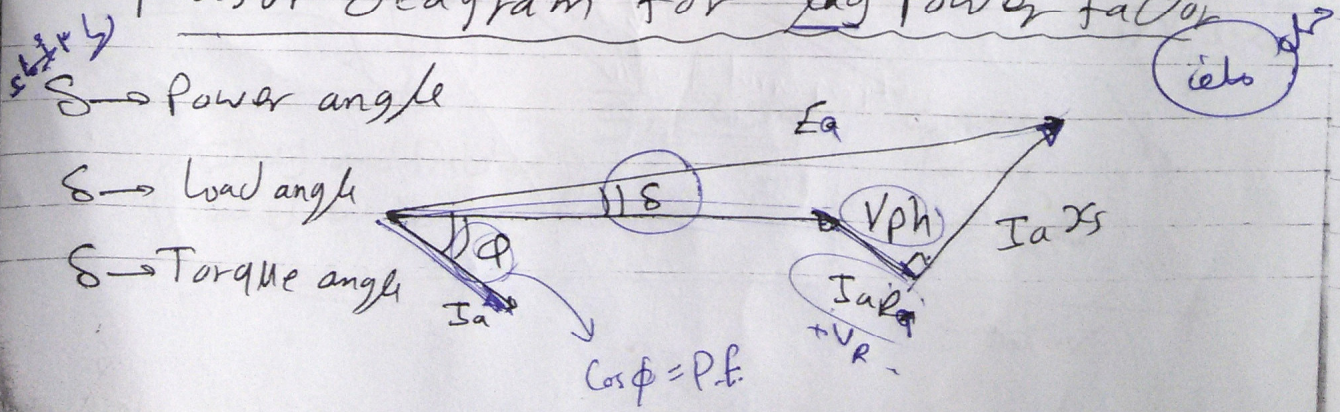

[4]


✓
phasor diagram for lead power factor

$\cos \phi$

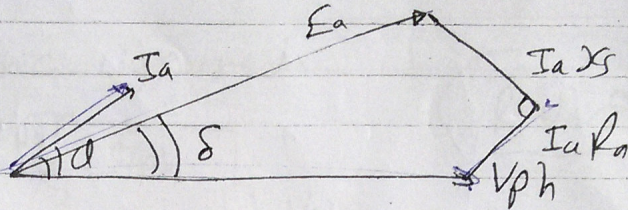

phasor diagram for unity power factor


$\cos \phi = 1$

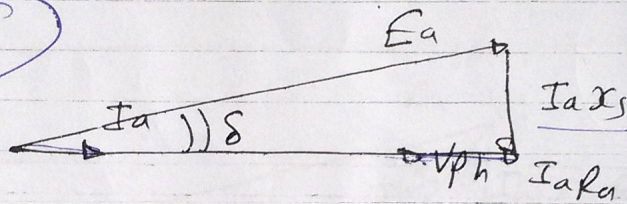

$$\% \text{ Voltage Regulation} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100$$


$$\% V.R = \frac{|E_a| - |V_{ph}|}{|V_{ph}|} \times 100$$

Power flow of synchronous generator

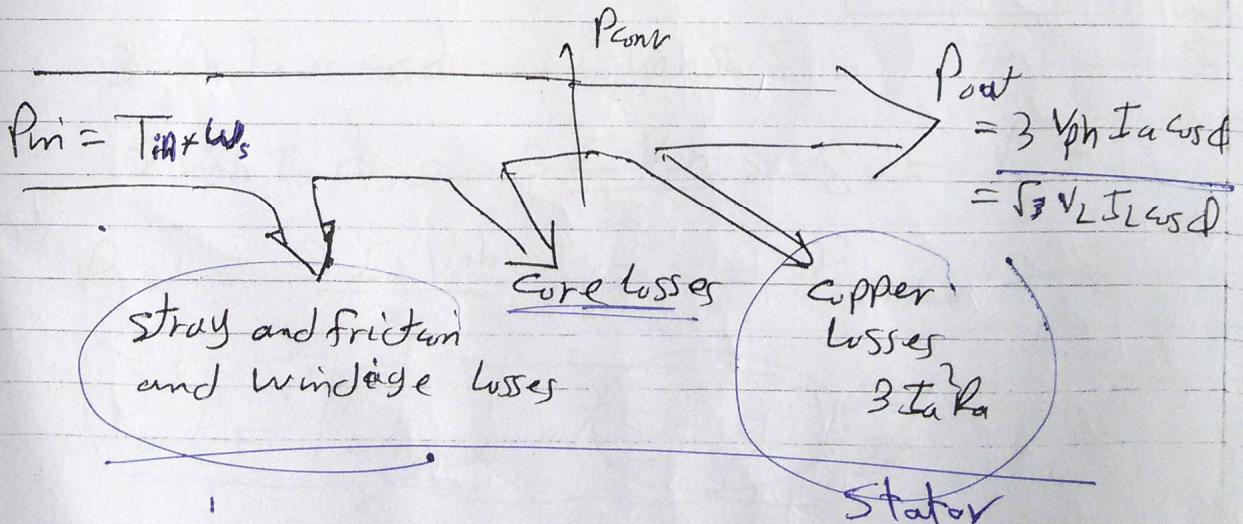


[5] ✓

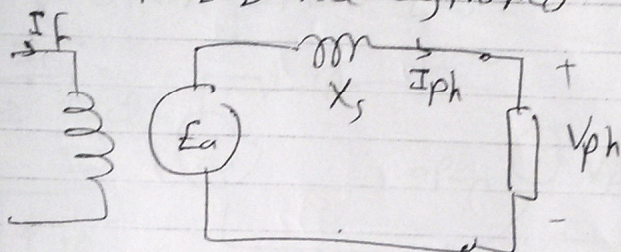Simplified phasor diagram with armature resistance ignored.



R_a is ignored

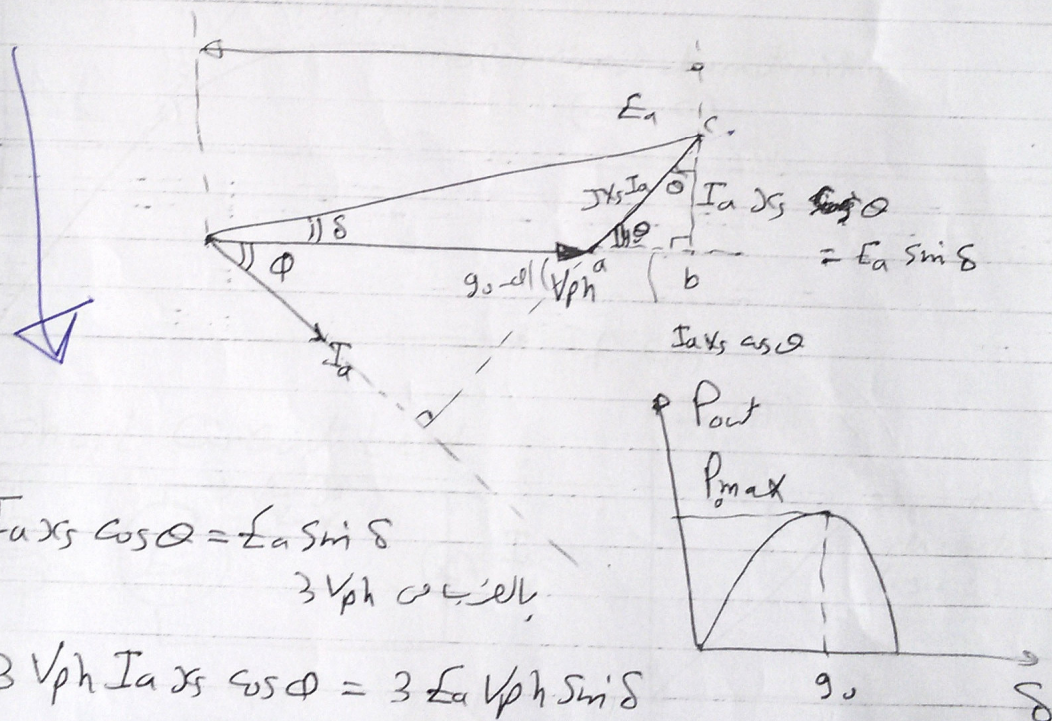

$$I_a X_s \cos \phi = E_a \sin \delta$$

$3 V_{ph} \cos \phi$

$$3 V_{ph} I_a \cos \phi = 3 E_a V_{ph} \sin \delta$$

$$3 V_{ph} I_a \cos \phi = \frac{3 E_a V_{ph}}{X_s} \sin \delta = P_{out}$$

$$P_{out} = \frac{3 E_a V_{ph}}{X_s} \sin \delta = P_{outmax} \sin \delta$$

$P_{out} = P_{outmax}$ at $\delta = 90^\circ$

The Conditions Required for Paralleling ✓

- 1 - The rms line voltages of the two generator must be equal.
- 2 - The two generators must have the same phase sequence.
- 3 - The phase angles of the two a phases must be equal.
- 4 - The frequency of the new generator, must be slightly higher than the frequency of the running system.

Starting synchronous Motors

ملاحظة

المحرك المتزامن لا يمكن تشغيله مباشرة، بل يجب أن يبدأ كحجم

1- Motor starting by Reducing Electrical frequency

2- Motor starting with an External primemover

3- Motor starting by using damper winding

Induction
Motor

تجده بعد كذا البند 5

